

Lab 5: Prelab

Students: Jing Ma, Muhammet Erkoc, Nelson Cortes

a). Voltage division

$$V_o(s) = \frac{V_s(s) \times \frac{1}{sC}}{R + \frac{1}{sC}}$$

$$\frac{V_o(s)}{V_s(s)} = \frac{1/sC}{sC \cdot R + 1} = \frac{1}{1 + sCR}$$

$$\rightarrow \frac{V_o(s)}{V_s(s)} = \frac{1}{1 + s\tau} \quad \# \tau = \text{time constant} = RC$$

$$\text{cutoff frequency, } f_c = \frac{1}{\tau} = \frac{1}{RC}$$

$$\therefore \omega_c = 2\pi f_c = \frac{2\pi}{RC} \text{ rad/sec}$$

b). First-order high pass filter
- Voltage division

$$V_o(s) = \frac{V_s(s) \times sL}{R + sL}$$

$$\frac{V_o(s)}{V_s(s)} = \frac{sL}{R + sL}$$

$$\frac{s(4R)}{\frac{R}{s} + \frac{4L}{s}} = \frac{s(4R)}{1 + s4R} \rightarrow \tau = 4R$$

$$f_c = \frac{1}{\tau} = \frac{R}{L}$$

$$\therefore \omega_c = 2\pi f_c = \frac{2\pi R}{L} \text{ rad/sec}$$